



# LOGISIM TUTORIALS



# Logic Gates

Building blocks of all digital circuits

AND

OR

NOT

XOR

# AND Gate

---

which only outputs a **1** if all inputs are **1**.

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

# OR Gate

---

which outputs a **1** if at least one input is **1**

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

# NOT Gate

---

inverts the input. If it's 0, it becomes 1, and if it's 1, it becomes 0.

A	Y
0	1
1	0

# XOR Gate

---

which outputs a 1 only when the inputs are different

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

A	B	C	Output (Light On/Off)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

---

# Three-Way Light Control Circuit

**Thank You**

